

Radio Frequency Circuits & Antenna

**Thomas Glezer
Tel Aviv University**

—

Homework: 8

May 25, 2022

1 A four-port network is characterized by the scattering matrix shown below:

$$\underline{\underline{S}} = \begin{pmatrix} 0.17 \exp(j90^\circ) & 0.63 \exp(-j45^\circ) & 0.68 \exp(-j45^\circ) & 0 \\ 0.63 \exp(-j45^\circ) & 0 & 0 & 0.56 \exp(j45^\circ) \\ 0.68 \exp(-j45^\circ) & 0 & 0.24 \exp(j38^\circ) & 0.38 \exp(j45^\circ) \\ 0 & 0.56 \exp(j45^\circ) & 0.38 \exp(-j45^\circ) & 0.32 \exp(-j32^\circ) \end{pmatrix} \quad (1)$$

a) Is this network loss-less?

$$|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 + |S_{41}|^2 = 0.17^2 + 0.63^2 + 0.68^2 = 0.8882 < 1 \quad (2)$$

Therefore, the network isn't lossless.

b) Is this network reciprocal?

$$S_{34} \neq S_{43} \quad (3)$$

Therefore, the network isn't reciprocal.

c) What is the return loss at port 1 when all other ports are matched?

$$RL = -20 \log |S_{11}| = -20 \log 0.17 = 15.39[dB] \quad (4)$$

d) What is the insertion loss and phase between ports 2 and 4, when all other ports are matched?

$$IL_{24} = -20 \log |S_{24}| = -20 \log 0.56 = 5.04[dB], \quad \varphi = 45^\circ \quad (5)$$

e) What is the reflection coefficient seen at port 1 if a short circuit is placed at the terminal plane of port 3, and all other ports are matched?

$$b_1 = S_{11}a_1 + S_{12}a_2 + S_{13}a_3 + S_{14}a_4 \quad (6)$$

$$b_3 = S_{31}a_1 + S_{32}a_2 + S_{33}a_3 + S_{34}a_4 \quad (7)$$

$$a_2 = a_4 = 0, a_3 = \rho b_3, \quad \rho = \frac{Z_l - Z_0}{Z_l + Z_0} \quad (8)$$

$$b_1 = S_{11}a_1 + S_{13}a_3 \quad (9)$$

$$b_3 = S_{31}a_1 + S_{33}a_3 \quad (10)$$

$$b_3 = S_{31}a_1 + S_{33}\rho b_3 \quad (11)$$

$$b_3(1 - S_{33}\rho) = S_{31}a_1 \quad (12)$$

$$a_3 = \rho b_3 = \frac{\rho S_{31}}{1 - S_{33}\rho} a_1 \quad (13)$$

Plugging (13) into (9):

$$b_1 = \left(S_{11} + \frac{\rho S_{31}}{1 - S_{33}\rho} \right) a_1 \quad (14)$$

$$(15)$$

When we short circuit $Z_l \rightarrow \infty, \rho \rightarrow -1$, then the reflection seen at port-1 is:

$$\frac{b_1}{a_1} = S_{11} - \frac{S_{31}}{1 + S_{33}\rho} \quad (16)$$

$$= 0.17j - \frac{0.68^2 \exp(-90^\circ)}{1.1891 + 0.1475j} \quad (17)$$

$$= 0.17j + \frac{0.4624}{1.1891 + 0.1475j} \cdot \frac{1.1891 - 0.1475j}{1.1891 - 0.1475j} \quad (18)$$

$$= 0.17j + \frac{0.4624(1.1891 - 0.1475j)}{1.1891^2 + 0.1475^2} \quad (19)$$

$$= 0.17j + 0.383 - 0.0475j \quad (20)$$

$$= 0.383 + 0.1225j \quad (21)$$

$$= 0.402 \angle 17.74 \quad (22)$$

2 A four-port network is characterized by the scattering matrix shown below:

$$\underline{\underline{\mathbf{S}}} = \begin{pmatrix} 0.17 \angle 139.2^\circ & 0.39 \angle 8.02^\circ & 0.67 \angle 91.07^\circ & 0.60 \angle -130.8^\circ \\ 0.39 \angle 8.02^\circ & 0.17 \angle 139.2^\circ & 0.67 \angle 91.07^\circ & 0.60 \angle 49.2^\circ \\ 0.67 \angle 91.07^\circ & 0.67 \angle 91.07^\circ & 0.30 \angle -30.58^\circ & 0.01 \angle 73.4^\circ \\ 0.60 \angle -130.8^\circ & 0.60 \angle 49.2^\circ & 0.01 \angle 73.4^\circ & 0.52 \angle 104.8^\circ \end{pmatrix} \quad (23)$$

The reference plane at port 3 is shifted outward at a distance of $\lambda/5$ and the reference plane at port 2 is shifted inward at a distance of $\lambda/6$ (λ is the wave length in the transmission line). Find the new scattering matrix of the network.

$$\tilde{\underline{\underline{\mathbf{S}}}} = \begin{pmatrix} 0.17 \angle 139.2^\circ & 0.39 \angle 68.02^\circ & 0.67 \angle 19.07^\circ & 0.60 \angle -130.8^\circ \\ 0.39 \angle 68.02^\circ & 0.17 \angle 259.7^\circ & 0.67 \angle 79.07^\circ & 0.60 \angle 109.2^\circ \\ 0.67 \angle 19.07^\circ & 0.67 \angle 79.07^\circ & 0.30 \angle -174.58^\circ & 0.01 \angle 1.4^\circ \\ 0.60 \angle -130.8^\circ & 0.60 \angle 109.2^\circ & 0.01 \angle 1.4^\circ & 0.52 \angle 104.8^\circ \end{pmatrix} \quad (24)$$

3 A four-port network is characterized by the scattering matrix shown below:

$$\underline{\underline{\mathbf{S}}} = \begin{pmatrix} 0.3 \angle -30^\circ & 0 & 0 & 0.8 \angle 0^\circ \\ 0 & 0.7 \angle -30^\circ & 0.7 \angle -45^\circ & 0 \\ 0 & 0.7 \angle -45^\circ & 0.7 \angle -30^\circ & 0 \\ 0.8 \angle 0^\circ & 0 & 0 & 0.3 \angle -30^\circ \end{pmatrix} \quad (25)$$

If ports 3 and 4 are connected by a lossless matched transmission line with an electrical length of 60° , find the resulting insertion loss and phase between ports 1 and 2.

$$a_2 = 0, \quad a_3 = Tb_4, \quad a_4 = Tb_3, \quad T = 1 \angle -60^\circ \quad (26)$$

$$b_1 = S_{11}a_1 + S_{14}Tb_4 \quad (27)$$

$$b_2 = S_{23}Tb_4 \quad (28)$$

$$b_3 = S_{33}Tb_4 \quad (29)$$

$$b_4 = S_{41}a_1 + S_{44}Tb_3 = S_{41}a_1 + S_{33}S_{44}T^2b_4 \quad (30)$$

$$b_4 = \frac{S_{41}}{1 - S_{33}S_{44}T^2}a_1 \quad (31)$$

$$b_2/a_1 = \frac{S_{23}S_{41}T}{1 - S_{33}S_{44}T^2} = \frac{0.7\angle -45^\circ \cdot 0.8 \cdot 1\angle -60^\circ}{1 - 0.7\angle -30^\circ \cdot 0.3\angle -30^\circ \cdot 1\angle -120^\circ} \quad (32)$$

$$= \frac{0.56\angle -105^\circ}{1 - 0.21\angle -180^\circ} = 0.463\angle -105^\circ \quad (33)$$

$$IL = -20 \log(0.463) = 6.69[dB], \quad \varphi = \arg(b_2/a_1) = -105^\circ \quad (34)$$

4 A two-port network is characterized by the scattering matrix shown below:

$$\underline{\underline{\mathbf{S}}} = \begin{pmatrix} \frac{1+j}{2} & \frac{1+j}{2} \\ \frac{1-j}{2} & \frac{1+j}{2} \end{pmatrix} \quad (35)$$

Is the network lossless?

$$S_{11}S_{12}^* + S_{21}S_{22}^* = 1/4[(1+j)(1-j) + (1-j)(1-j)] = 1/4[1 + 1 + 1 - 2j - 1] = 1/2(1-j) \neq 0$$

Therefore, the network isn't lossless.

5 Two identical reciprocal and lossless two-port networks are connected by a lossless transmission line of length l (see Figure 1). The propagation constant of the line is β and characteristic impedance is Z_0 . Every two-port network is represented as shunt element $Y = jb$. The characteristic impedance of the ports is Z_0 .

- a) Find the scattering matrix element S_{11} of the system consisting of the two two-ports networks and the transmission line.

The shunt element matrix can be presented like:

$$\underline{\underline{\mathbf{S}}} = \begin{pmatrix} 1 & 0 \\ jb & 1 \end{pmatrix} \quad (36)$$

The transmission line section matrix can be presented like:

$$\underline{\underline{\mathbf{S}}} = \begin{pmatrix} \cos \theta & jZ_0 \sin \theta \\ jY_0 \sin \theta & \cos \theta \end{pmatrix}, \quad \theta = \beta l \quad (37)$$

The ABCD matrix of the equivalent circuit can be find in the next way:

$$\begin{pmatrix} A & B \\ C & D \end{pmatrix} = \begin{pmatrix} 1 & 0 \\ jb & 1 \end{pmatrix} \begin{pmatrix} \cos \theta & jZ_0 \sin \theta \\ jY_0 \sin \theta & \cos \theta \end{pmatrix} \begin{pmatrix} 1 & 0 \\ jb & 1 \end{pmatrix} \quad (38)$$

$$\begin{pmatrix} A & B \\ C & D \end{pmatrix} = \begin{pmatrix} 1 & 0 \\ jb & 1 \end{pmatrix} \begin{pmatrix} \cos \theta - bZ_0 \sin \theta & jZ_0 \sin \theta \\ j[Y_0 \sin \theta + b \cos \theta] & \cos \theta \end{pmatrix} \quad (39)$$

$$\begin{pmatrix} A & B \\ C & D \end{pmatrix} = \begin{pmatrix} \cos \theta - bZ_0 \sin \theta & jZ_0 \sin \theta \\ j[Y_0 \sin \theta + 2b \cos \theta - Z_0 b^2 \sin \theta] & \cos \theta - bZ_0 \sin \theta \end{pmatrix} \quad (40)$$

$$S_{11} = \frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D} \quad (41)$$

$$S_{11} = \frac{\cos \theta - Z_0 b \sin \theta + j(\sin \theta - 2bZ_0 \cos \theta + (Z_0 b)^2 \sin \theta - \sin \theta) - \cos \theta + Z_0 b \sin \theta}{2(\cos \theta - Z_0 b \sin \theta) + j[2 \sin \theta + 2bZ_0 \cos \theta - (Z_0 b)^2 \sin \theta]} \quad (42)$$

$$S_{11} = \frac{j((Z_0 b)^2 \sin \theta - 2bZ_0 \cos \theta)}{2(\cos \theta - Z_0 b \sin \theta) + j[2 \sin \theta + 2bZ_0 \cos \theta - (Z_0 b)^2 \sin \theta]} \quad (43)$$

- b) Find the length l of the transmission line section for which $|S_{11}| = 0$ and express it using Z_0, b, β .

$$S_{11} = 0 \quad (44)$$

$$(Z_0 b)^2 \sin \theta - 2bZ_0 \cos \theta = 0 \quad (45)$$

$$Z_0 b \sin \theta - 2 \cos \theta = 0 \quad (46)$$

$$\tan \theta = \frac{2}{Z_0 b} \quad (47)$$

$$l = 1/\beta \arctan \frac{2}{Z_0 b} \quad (48)$$